

**EXPERIMENT 10: SINGLE-TRANSISTOR AMPLIFIERS**


5/9/06

In this experiment we will measure the characteristics of common emitter and common collector amplifiers. We will use the 2N3904 npn transistor.

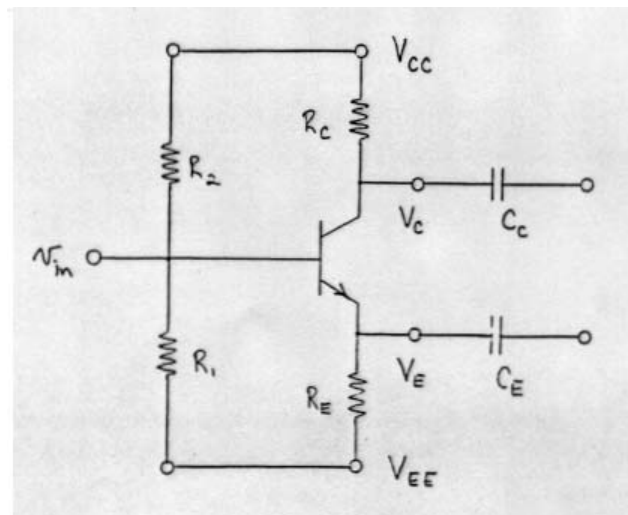**I. THE COMMON EMITTER AMPLIFIER**

The common emitter amplifier has a moderate gain as well as moderate input and output impedances. The circuit we will use is shown below. In this circuit resistors  $R_1$  and  $R_2$  are used to set the base to the desired DC operating voltage. Often in circuits of this kind, one uses an input capacitor to decouple the DC voltage level of  $v_{in}$  from the base. In the present circuit what we do instead is adjust  $V_B$  to match the DC level of the source, thus making the capacitor unnecessary. The output of the amplifier is taken from the collector through capacitor  $C_c$ , so that  $v_{out}$  has a DC level of zero.

The resistor  $R_E$  provides negative feedback in the following way. If the base voltage  $V_B$  is raised,  $I_B$  and  $I_E$  both increase. As more current flows through  $R_E$ , the emitter voltage also rises (since  $V_E = V_{EE} + I_E R_E$ ). This prevents  $V_{BE}$  from changing by very much, which in turn means that the changes in  $I_E$  will not be too large. If one chooses a small value for  $R_E$  the gain of the amplifier will be large, but the amplified signal will be distorted and sensitive to changes in temperature.



## TRANSISTOR AMPLIFIERS

Before you come to lab, you should complete the homework problems (problems 8.7 and 8.8 in Sprott) that involve designing and calculating the properties of a common emitter amplifier. .

1. The circuit we will use is mounted on a pre-wired circuit board. Sketch the circuit in your lab notebook, labeling the values of all components including the precision of all resistors used in the circuit. The value of  $C_C$  is not apparent from the markings on the capacitor and will be measured in step 5 below.
2. Use the transistor curve tracer to obtain the collector characteristics for your transistor and place a fully labeled printed copy in your lab notebook.
3.
  - (a) Install the transistor in the circuit board. Connect the power supplies for  $V_{CC}$  and  $V_{EE}$  and then set  $V_{CC} = +20$  V, and  $V_{EE} = -1.5$  V. For now, the function generator ( $v_{in}$ ) should not be connected. Using a DMM, adjust  $V_{EE}$  to get  $V_B$  to within 1 mV of zero. Then measure  $V_{EE}$ ,  $V_C$ , and  $V_E$  (with the DMM) and calculate the quiescent (DC) value of  $I_C$ .
  - (b) Draw the load line on your copy of the transistor characteristics, and mark the DC operating point. Determine  $I_B$  at the operating point (from the plot) and find  $\beta$ .
  - (c) Calculate  $r_{tr}$ ,  $r_{in}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G$ , and the values of  $V_C$  at cutoff ( $I_C = 0$ ) and at saturation ( $V_{CE} = 0.3$  V).
4.
  - (a) Set up the function generator to produce sine waves with frequency  $f = 10$  kHz. Install a  $4.7\ \Omega$  resistor across the terminals of the function generator and connect it between the base and ground. Adjust the amplitude of  $v_{in}$  to obtain an AC voltage of 2 V (RMS) at the collector (use a DMM). Make a sketch of  $v_{in}$  and the voltage at the collector (remember that the collector voltage has both AC and DC parts).
  - (b) Use a DMM to measure  $v_{in}$  and  $v_{out}$  and calculate the open circuit (noload) gain,  $G_0$ . Compare your result with the calculated value of  $G$ .
  - (c) Measure  $R_{in}$  and  $R_{out}$ , and compare your results with the calculate values. To measure  $R_{in}$ , put a resistor  $R$  between the function generator and the base and adjust  $R$  until  $V_B$  (or  $v_{out}$ ) drops by a factor of 2 (see Lab #1, step 5). To measure  $R_{out}$  use the procedure of Lab #3, step 2(c), with the resistor on the output side of  $C_C$ .

## TRANSISTOR AMPLIFIERS

(if you were to connect the resistor on the collector side of  $C_C$  you would change the DC operating point of the amplifier)

5. (a) Connect a load resistor  $R_L = 3000 \, \Omega$  between the output and ground. Using a DMM, measure and tabulate  $v_{in}$  and  $v_{out}$  as a function of frequency for  $20 \text{ Hz} \leq f \leq 50 \text{ kHz}$  (3 points/decade is sufficient except near the corner frequency). Plot the gain as a function of  $f$  on log-log paper.
- (b) The falloff in the gain at low frequencies is caused by the non-zero impedance of the output capacitor. From your graph determine the breakpoint frequency (i.e. the frequency at which  $G$  has dropped off by a factor of  $\sqrt{2}$  compared to the high-frequency limit). At this frequency, the voltage across  $C_C$  is equal in magnitude to the voltage across the output resistors; i.e.,

$$|Z_C| = R_L + R_{out}.$$

Use this formula together with your measured breakpoint frequency to determine  $C_C$ .

6. Remove  $R_L$ , set the function generator to  $f = 10 \text{ kHz}$ , and increase  $v_{in}$  to drive  $v_C$  to both cutoff and saturation (you may need to remove the  $4.7 \, \Omega$  resistor for this step). Sketch the collector voltage and determine  $V_C(\text{off})$  and  $V_C(\text{sat})$ . Compare your measured and calculated values.
7. In this step we will observe the behavior of the amplifier in the “grounded-emitter” configuration. Rather than grounding the emitter directly, the idea is to “bypass”  $R_E$  by connecting the capacitor  $C_E$  to ground. This keeps the DC operating point of the amplifier unchanged, while grounding the emitter as far as AC voltages are concerned. In other words, the emitter voltage will now be constant, which means that there is no longer any negative feedback.
- (a) Connect  $C_E$  to ground and adjust the amplitude of  $v_{in}$  to obtain  $v_{out} = 5 \text{ V}$  peak-to-peak (you will need to put the  $4.7 \, \Omega$  resistor, back in). Use a DMM to measure the magnitude of  $v_{in}$  and  $v_{out}$ , and determine the open-circuit gain. For grounded-emitter operation the gain is given by  $G = R_C/r_{tr}$ . Use the measured value of  $G$  to determine the transresistance and compare your result with the expected value

$$r_{tr} = V_{kT}/I_E.$$

- (b) Switch the function generator to triangle waves and increase  $v_{out}$  to  $8 \text{ V}$  peak-to-peak. Make a sketch of the collector voltage,  $v_C(t)$ , including both the DC and AC parts. On the same graph, indicate the quiescent value of  $v_C$  (i.e. the value obtained with  $v_{in} = 0$ ). Can you explain why  $v_C$  looks the way it does?
- (c) Measure the input impedance. Compare your result with the expected value of  $R_{in}$  calculated with the measured value of  $r_{tr}$ .

## II. THE COMMON COLLECTOR AMPLIFIER

The common collector amplifier has a gain of approximately 1, a moderate input impedance, and a very low output impedance. We will use the same circuit as above, with the output taken from the emitter.

1. Set the function generator frequency to  $f = 10 \text{ kHz}$ . Adjust the amplitude of  $v_{in}$  to obtain an RMS emitter voltage of approximately 0.25 V. Sketch  $v_{in}$  and  $v_E$ , remembering to include both the AC and DC parts. Measure the gain (use a DMM) and compare your result with calculated value (use the measured value of  $r_{tr}$  in the calculation).
2. The final step is to measure the output impedance of the amplifier. Use the following procedure. First, remove the  $4.7 \text{ } \Omega$  resistor and then put a  $100 \text{ k}\Omega$  resistor in series with the function generator. Using a DMM, check that  $V_B$  is zero to within 1 mV, and if not, adjust  $V_{EE}$  to zero  $V_B$ . Next adjust the amplitude of  $v_{in}$  to obtain  $v_E = 0.1 \text{ V (RMS)}$ . Connect a load resistor  $R_L$  between the output side of  $C_E$  and ground, and then adjust  $R_L$  to obtain  $v_{out} = v_B/2$  (here  $v_{out}$  is the voltage across  $R_L$ ). At this point  $R_L = R_{out}$ . Note that as you adjust  $R_L$ , both  $v_{out}$  and  $v_B$  change. As a result, you need to measure both  $v_{out}$  and  $v_B$  as you adjust  $R_L$ .