

Comp 182 Chapter 3


Digital Logic Level

Gates

And, Or, Not

Nand, Nor

How they are created.

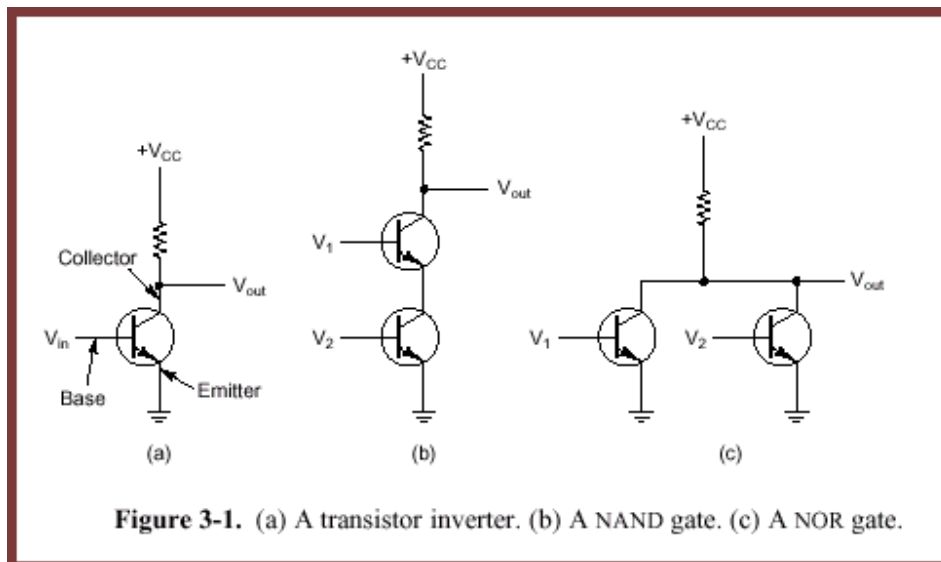

The inverter is a Not. Typically the Not, Nand, Nor gates are used as the basic building blocks because they can be created with fewer transistors.

If an and gate is required - for example - it can be created by tying a a Nand to a Not.

Boolean Algebra - Nomenclature.


If we designate A and B as inputs to a gate, and X as the output we write:

$AB = X$ for A And B = X

$A+B = X$ for A Or $B = X$

$\overline{AB} = X$ for $Not (AB) = X$

Symbols

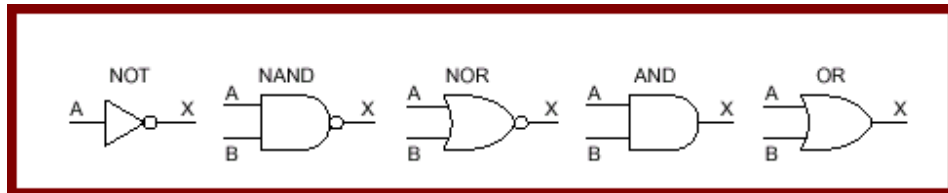

Truth Tables

<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table> <p>Not</p>	A	X	0	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <p>Nand</p>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> <p>Nor</p>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <p>And</p>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> <p>Or</p>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	X																																																																					
0	1																																																																					
1	0																																																																					
A	B	X																																																																				
0	0	1																																																																				
0	1	1																																																																				
1	0	1																																																																				
1	1	0																																																																				
A	B	X																																																																				
0	0	1																																																																				
0	1	0																																																																				
1	0	0																																																																				
1	1	0																																																																				
A	B	X																																																																				
0	0	0																																																																				
0	1	0																																																																				
1	0	0																																																																				
1	1	1																																																																				
A	B	X																																																																				
0	0	0																																																																				
0	1	1																																																																				
1	0	1																																																																				
1	1	1																																																																				

Truth Tables

Identities

These are the rules of boolean algebra - similar to the rules of normal algebra. Eg. in normal algebra $A \times B = B \times A$, but $A - B \neq B - A$.

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

Figure 3-6. Some identities of Boolean algebra.

Given these identities, with a bit of thought it can be seen that there is more than one way to accomplish the same truth-table.



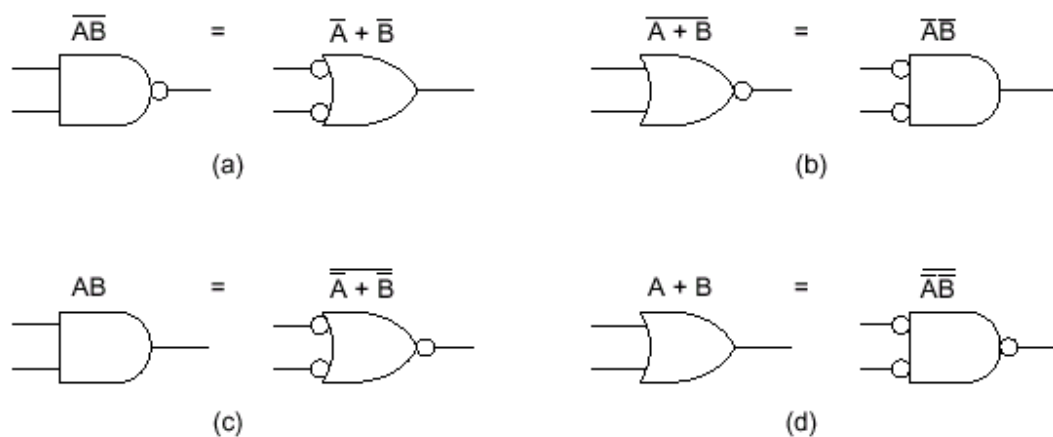
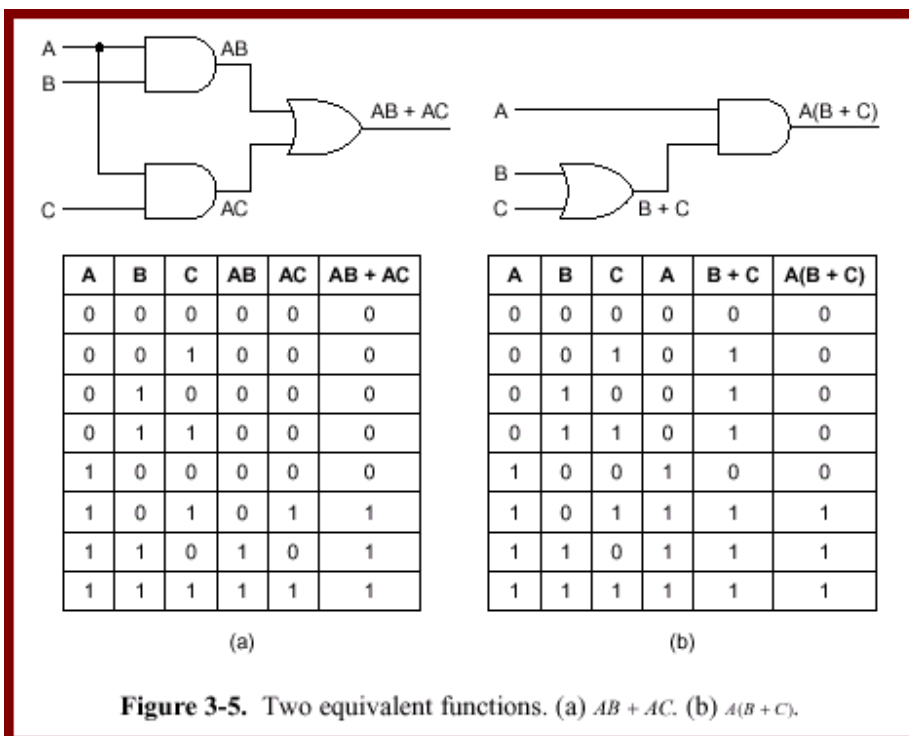


Figure 3-7. Alternative symbols for some gates: (a) NAND. (b) NOR. (c) AND. (d) OR.

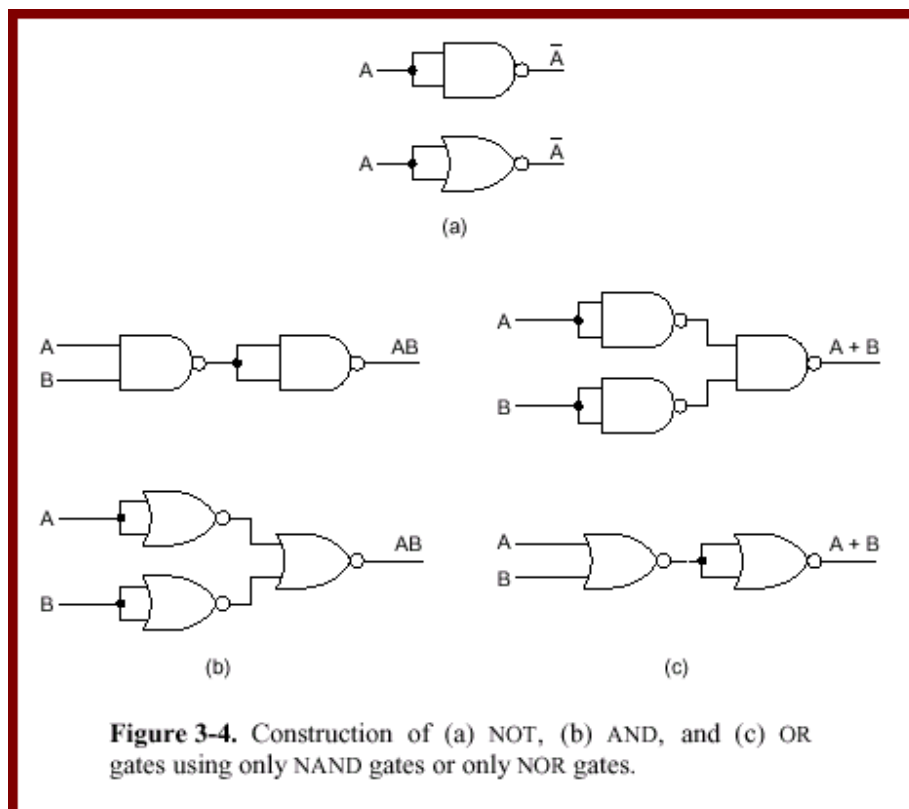


XOR

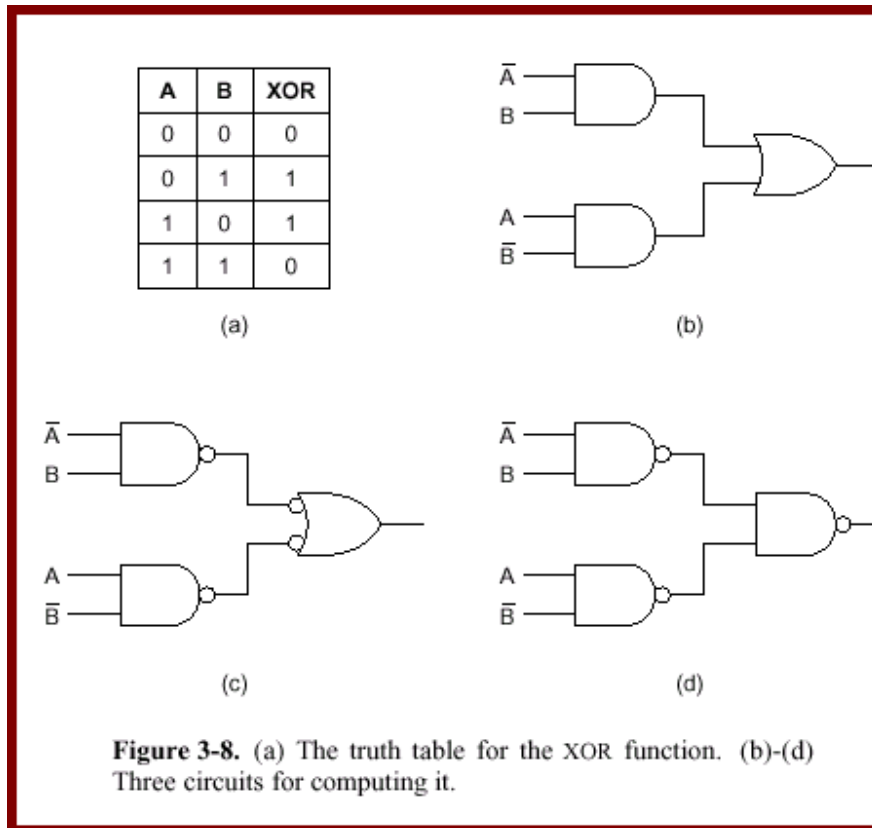


Basic Digital Logic Circuits

Combinational Circuits

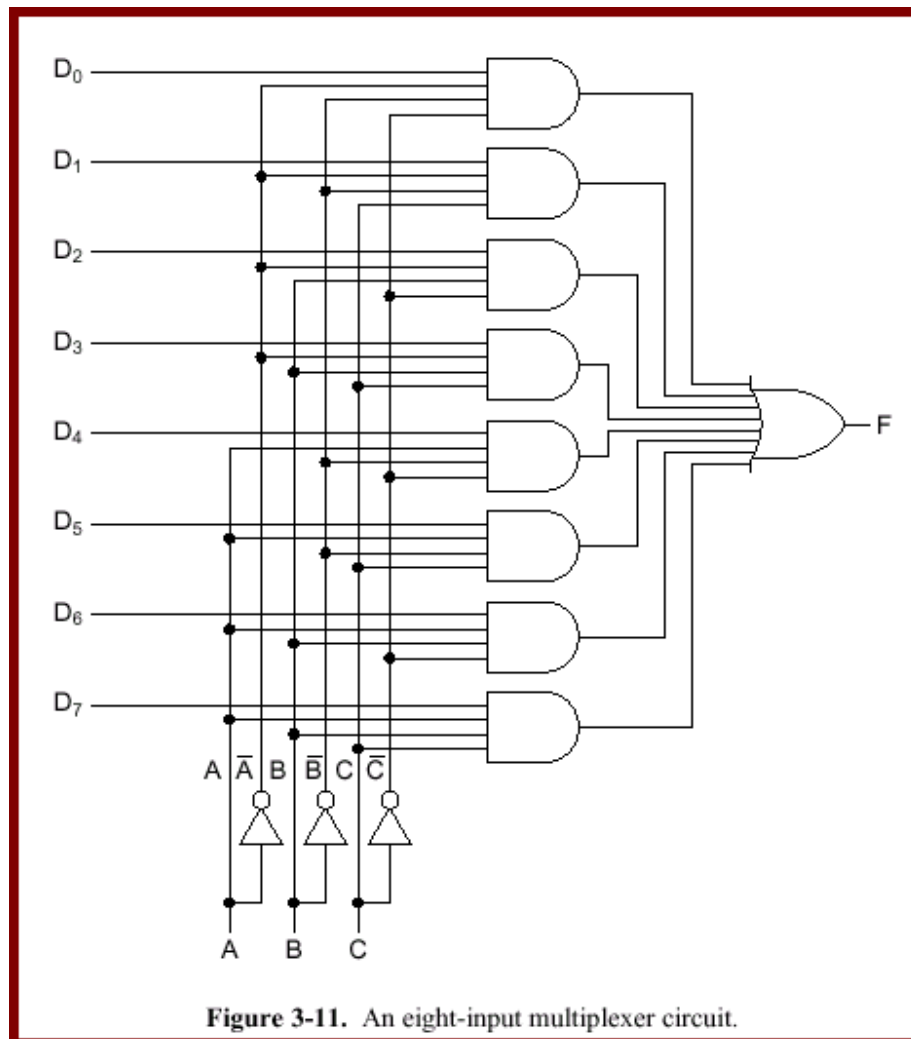
- Multiplexers - Selects one of n inputs.



- **Decoders - Sets one of n outputs.**

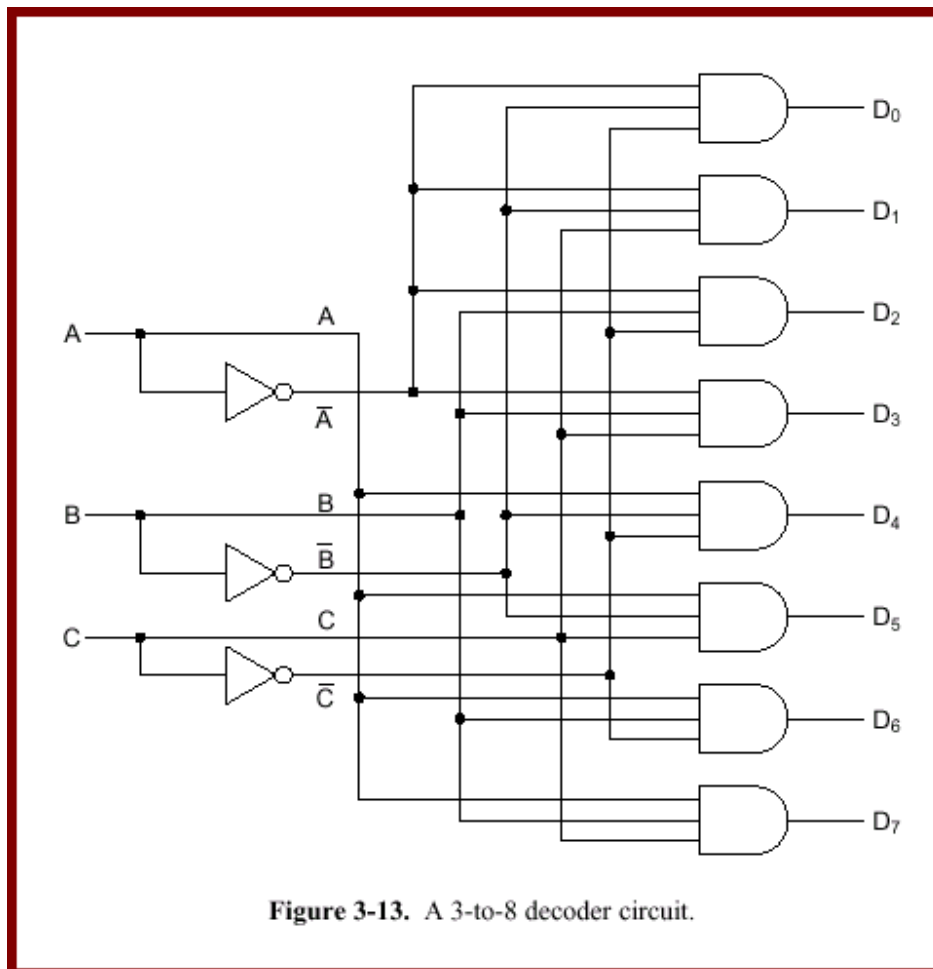


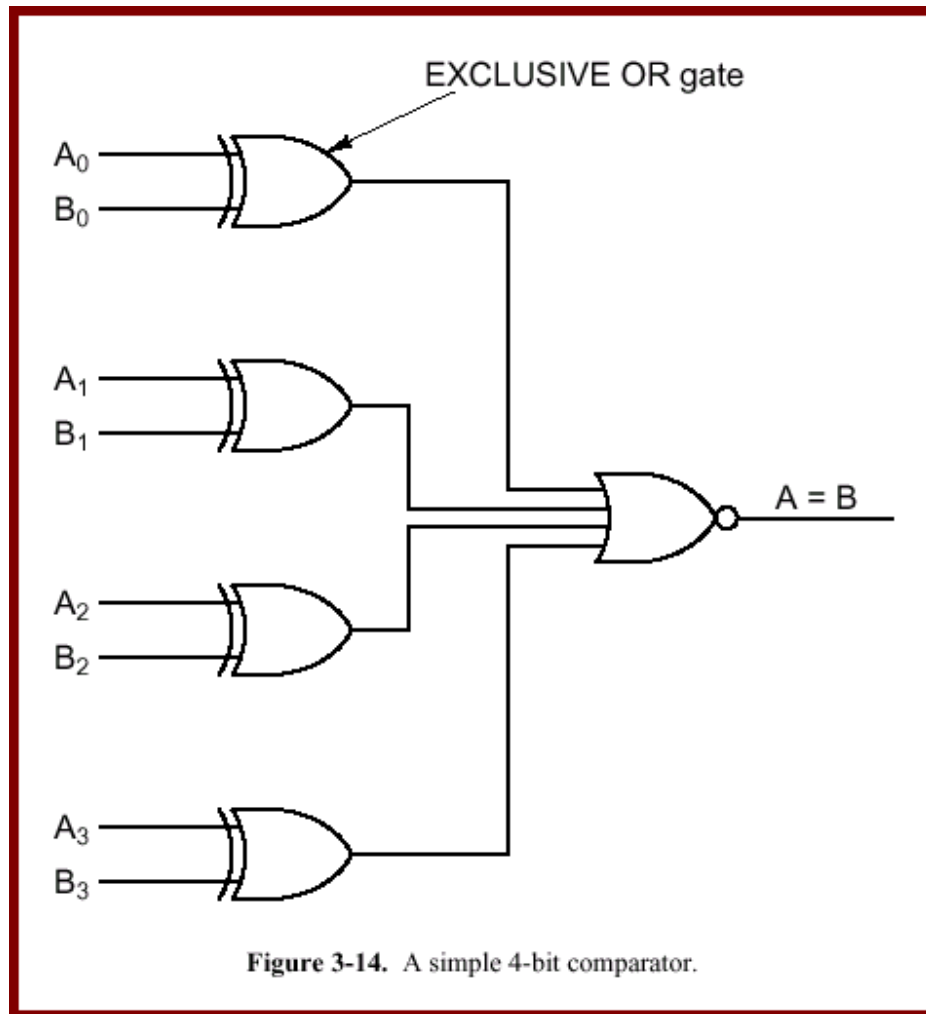- **Comparators - Are the inputs the same?**





Arithmetic circuits

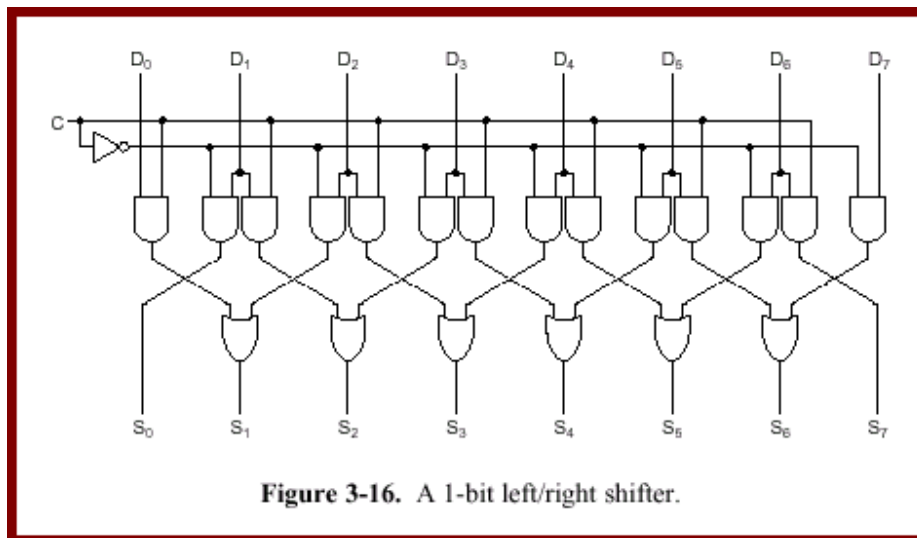- Shifters - Move a bit left or right (multiply/divide by 2).



- **Adders - Add the bits together.**

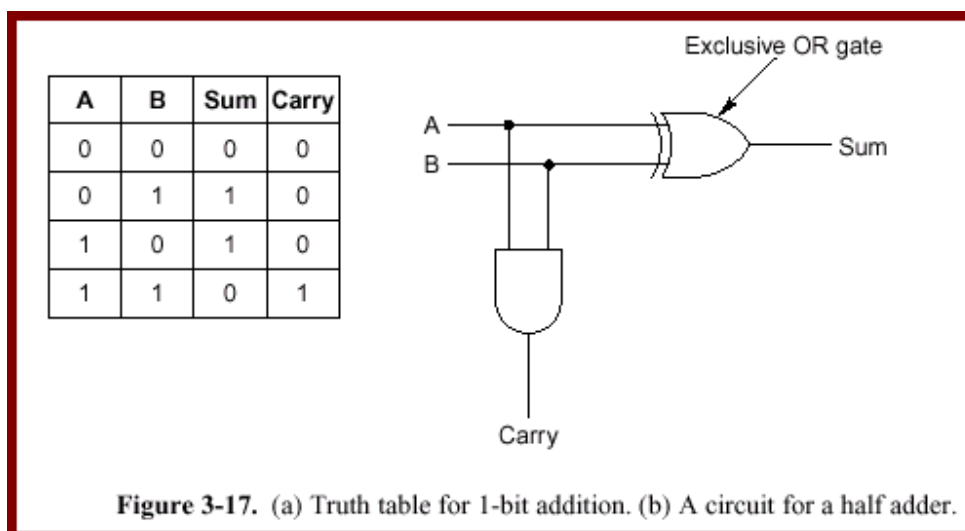

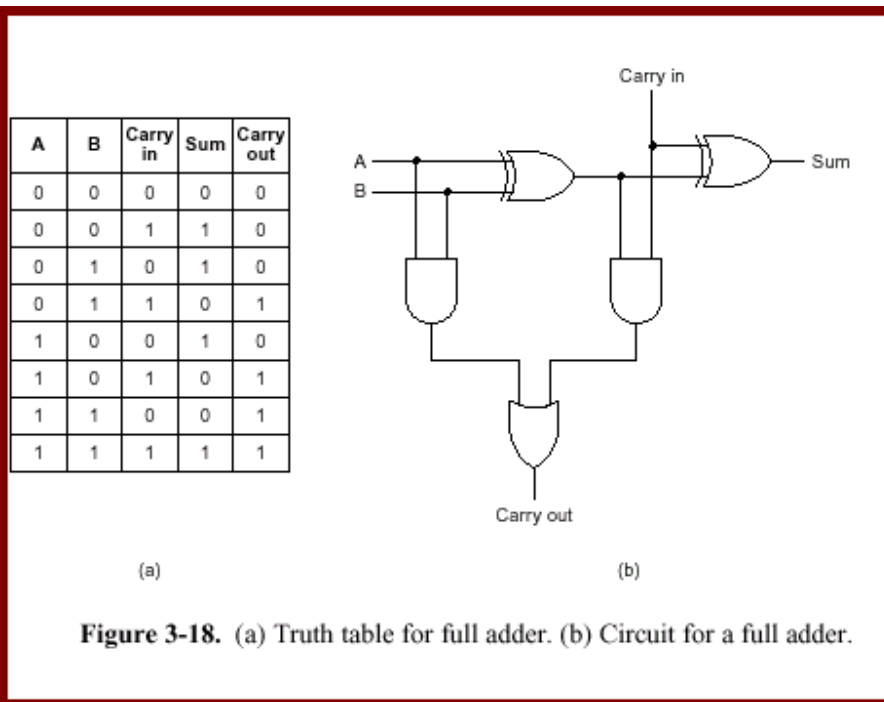

- ALU's


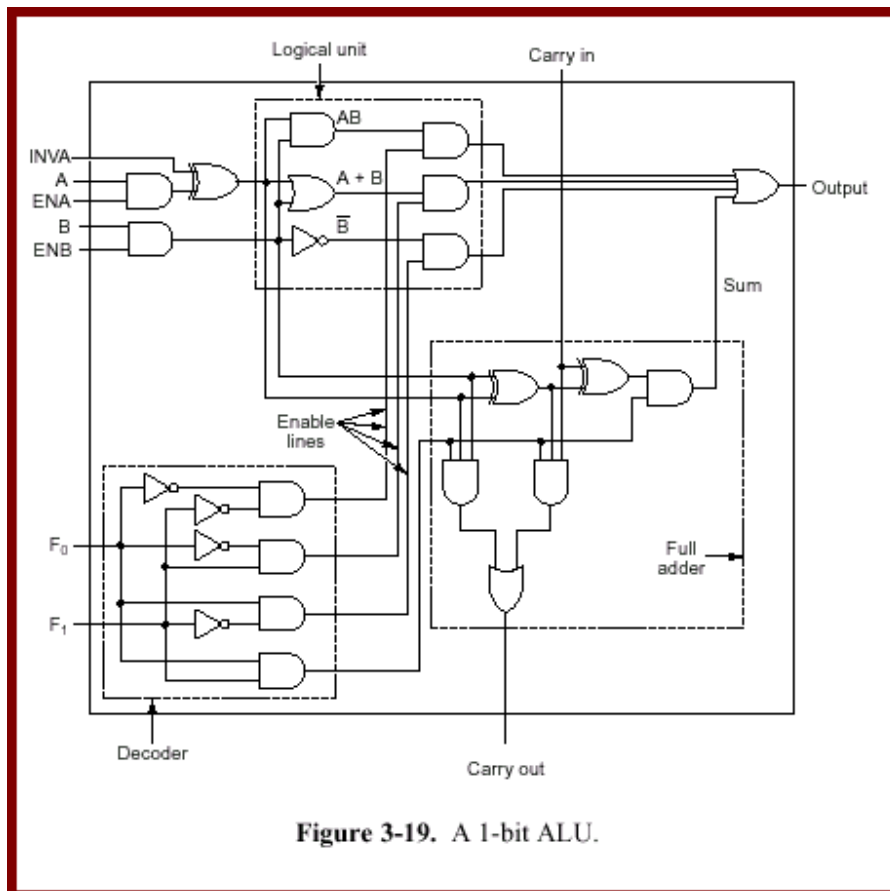



Figure 3-19. A 1-bit ALU.

- **Clocks - When to do it.**


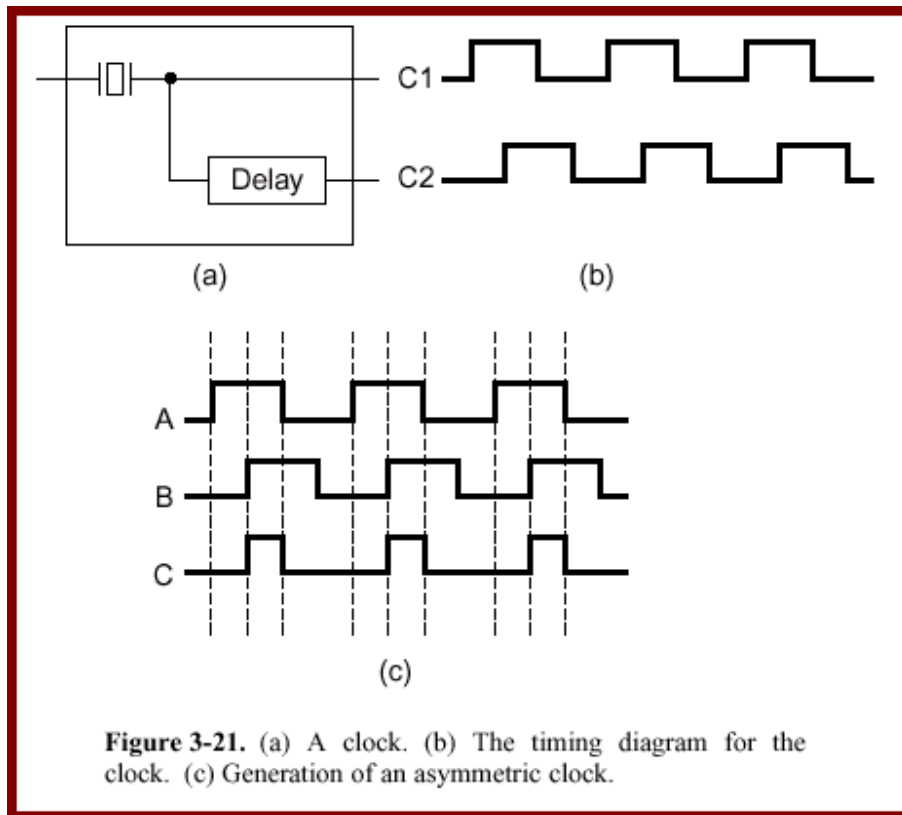


Memory


- Latches - switched on input value

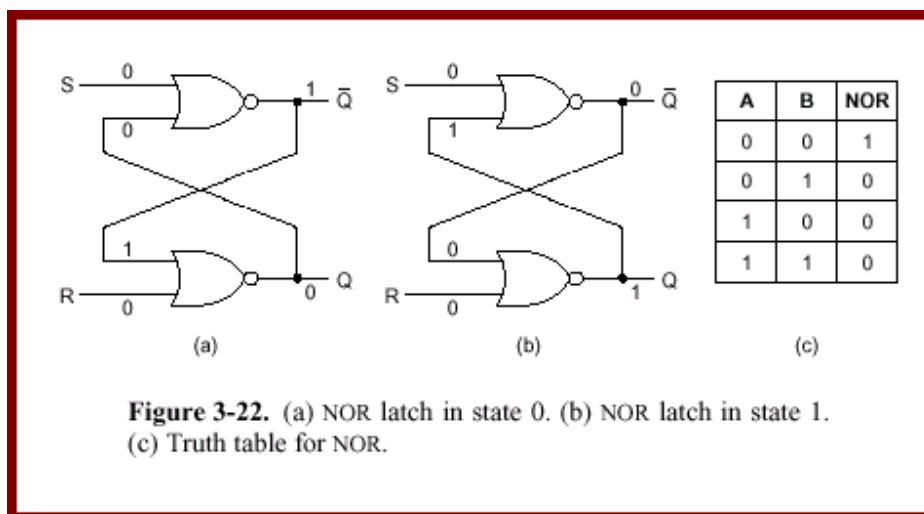

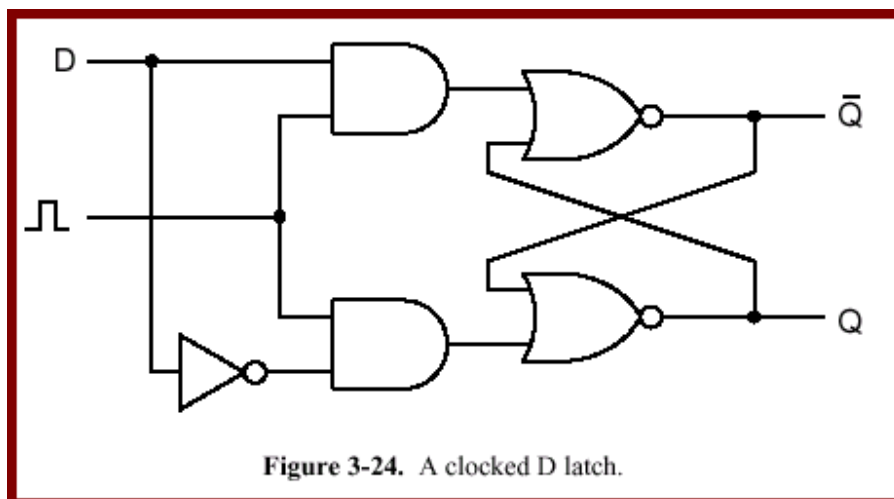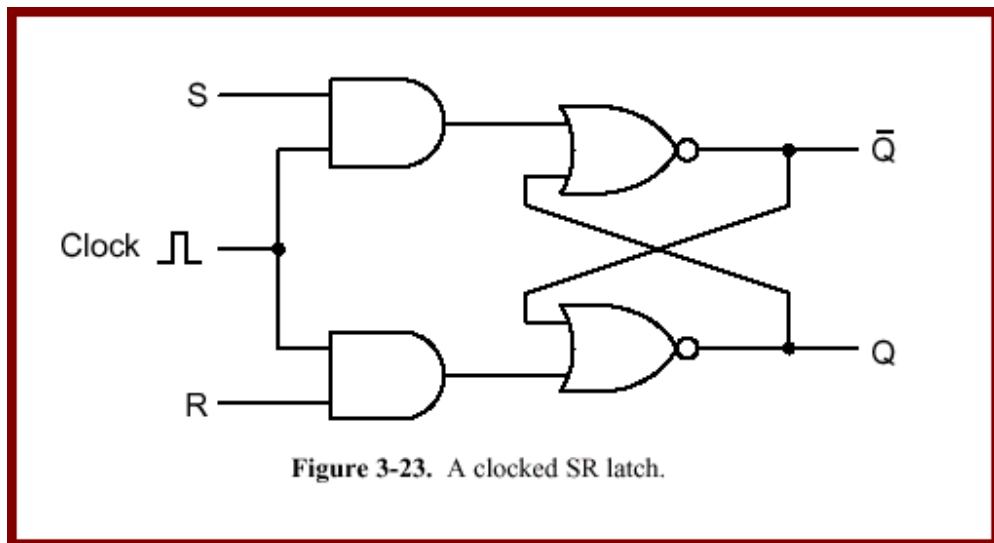
- Clocked Latches set to input value when clocked



- Rising/falling pulse

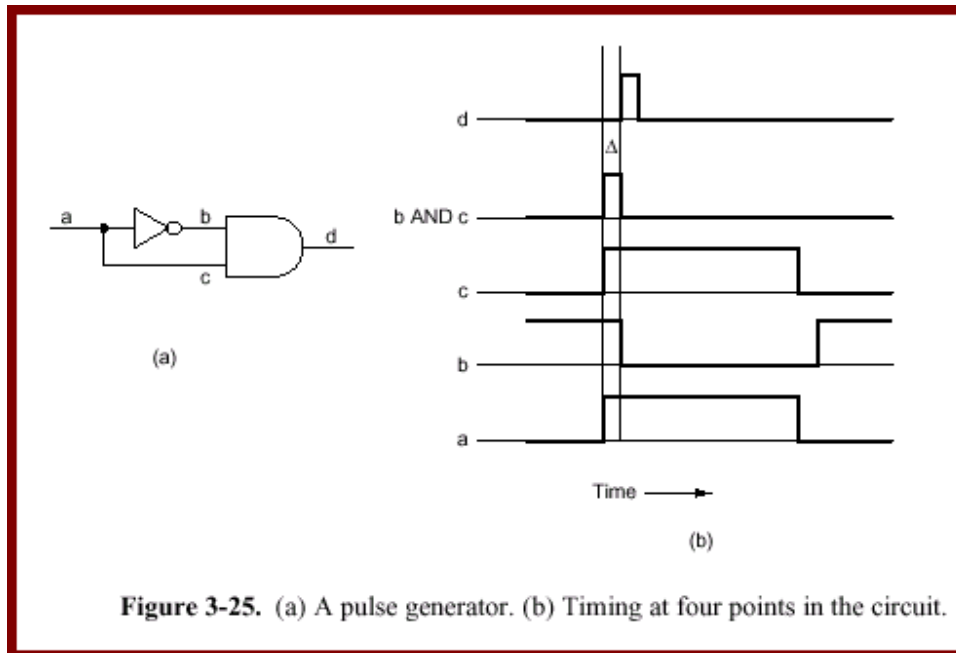

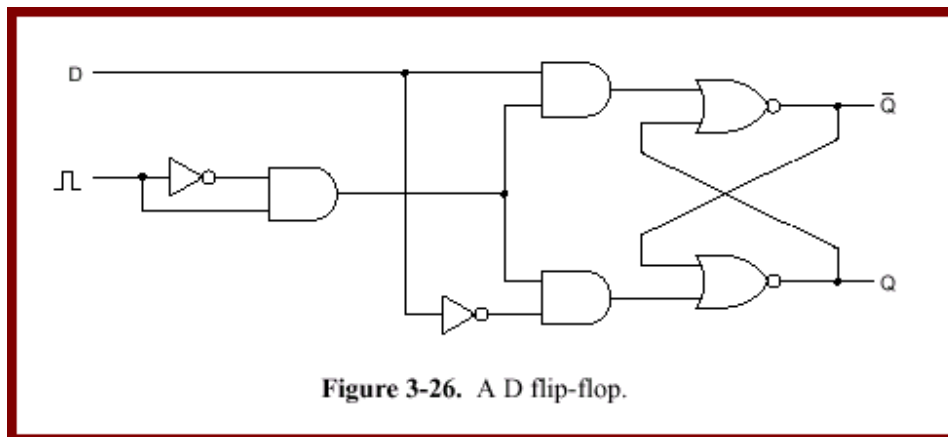- **Flip-Flops set on rising or falling pulse**



- **Registers**

Memory Organization

RAM, ROM

Integrated circuits - Some Real *Texas Instruments* Products


[4 Nand gates](#)

SN5401, SN54LS01,

SN7401, SN74LS01

QUADRUPL 2-INPUT POSITIVE-NAND GATES WITH OPEN-COLLECTOR OUTPUTS

logic diagram (positive logic)

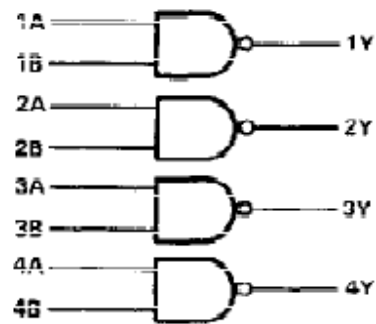


positive logic: $Y = \overline{A \cdot B}$ or $Y = \overline{A} + \overline{B}$

[Multiplexer](#)

SN54ALS151, SN74ALS151, SN74AS151 **1-OF-8 DATA SELECTORS/MULTIPLEXERS**


SDAS205A—APRIL 1982—REVISED DECEMBER 1994

logic symbol†

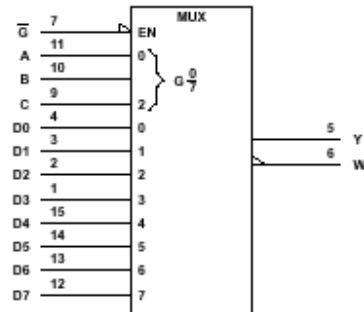

† This symbol is in accordance with ANSI/IEEE Std 91-1984 and IEC Publication 617-12. Pin numbers shown are for the D, J, and N packages.

logic diagram (positive logic)

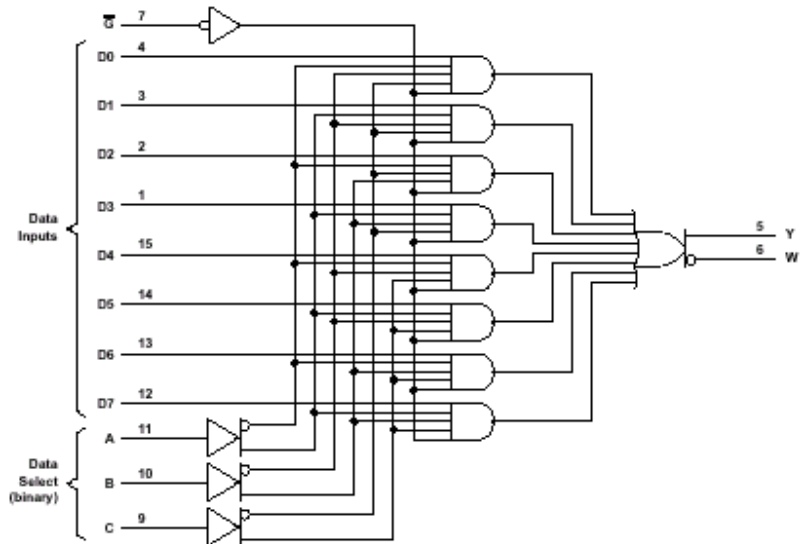


Pin numbers shown are for the D, J, and N packages.




SN54AHC138, SN74AHC138 **3-LINE TO 8-LINE DECODERS/DEMULTIPLEXERS**

SCLS258G – DECEMBER 1995 – REVISED JULY 1998


logic diagram (positive logic)

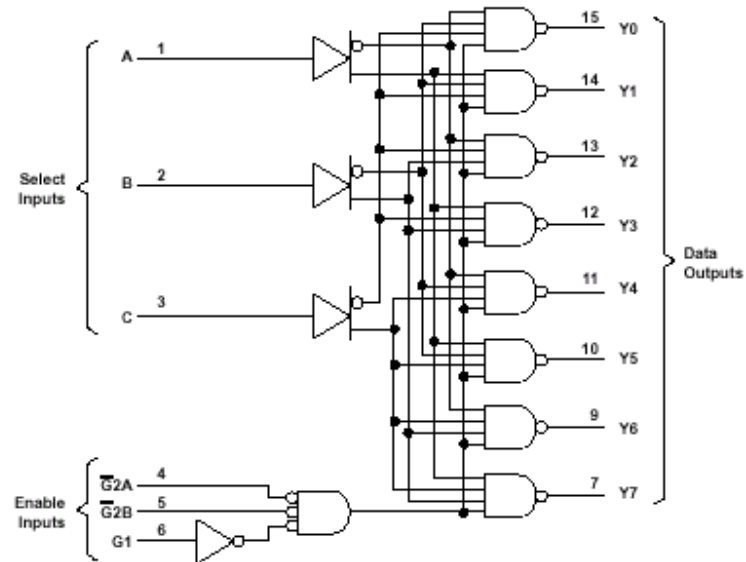

CPU Chips

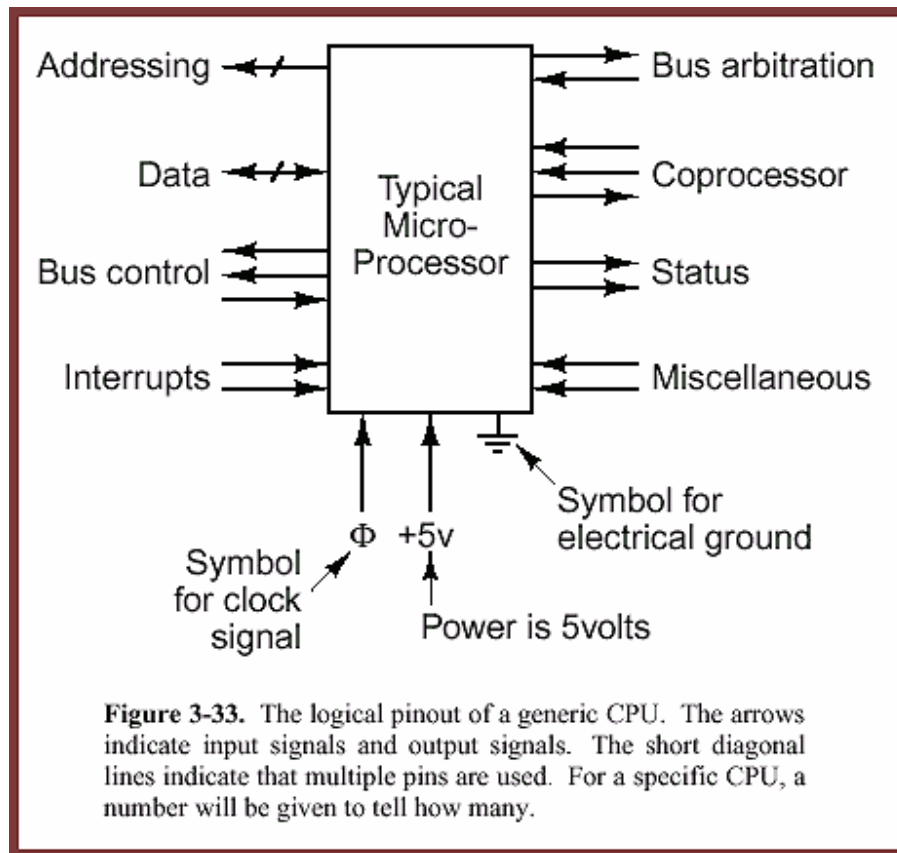

Buses

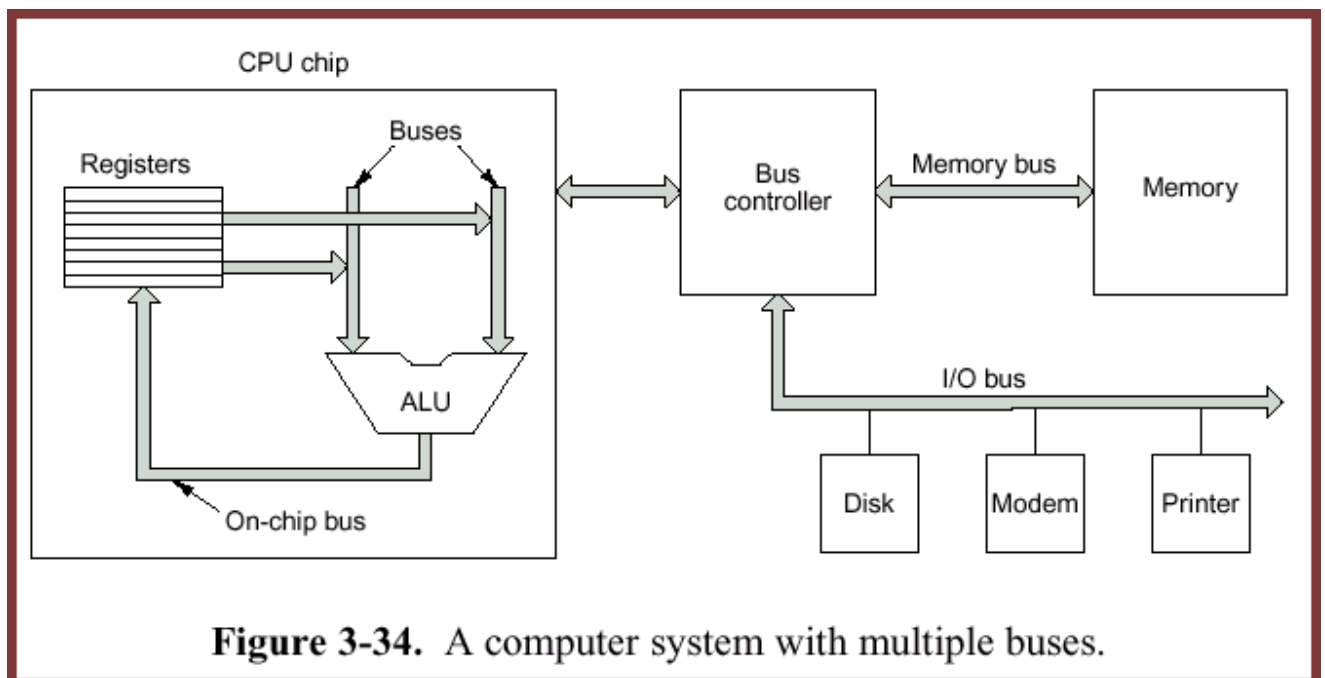

Width

Clocking - speed

Synchronous

Asynchronous

Arbitration

Interrupts

Example CPU Chips

- Pentium II
 - UltraSPARC II
 - picoJava II
-

Example Buses

ISA

PCI

USB

Interfacing

I/O Chips

PIO - 8255

Address Decoding