

Physics 623
Digital Circuits I and II
Nov. 17, 1999

Digital Circuits I

1 Purpose

- To introduce the basic principles of digital circuitry.
- To understand the small signal response of various gates and circuits typical of the currently available TTL integrated circuitry.

2 Discussion

The circuits are TTL 7400 series of various types from various manufacturers. Use the built-in supply for $V_{cc} = +5$ V DC. The logic levels are:

- **One:** 3 to 5.0 volts; nominally 4.75 V.
- **Zero:** 0 to 0.4 volts; nominally ground = 0 V.
- Switching Level ~ 1.4 V.

The delay in passing a signal through one NAND gate is typically 13 ns for the SN7400 series and is about 7 ns for the 74LS00 series. The fanout capability is 10, (i.e. ten inputs can be connected to each output). The operating temperature range is from about 0°C to 70°C. The general characteristics of TTL logic are described in the attached sheets together with the detailed specifications of individual chips.

Every input of every logical unit you use **must** be connected to something. Check each input pin around the symbol on the data sheet and decide where it should be connected. They are not always indicated on the simplified logic diagrams.

3 Procedure

1. Verify the truth table for a two input NAND gate.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

2. Use 2 input NAND gates to implement the logic values shown below. Use DeMorgan's theorem, if necessary. Use the switches and/or push buttons on your breadboard for inputs and the LED indicators to show the output states.

- (a) A 2 input AND gate.

$$Y = A \cdot B$$


- (b) A 2 input exclusive OR

$$Y = A \oplus B \text{ or equivalently } Y = A \cdot \bar{B} + \bar{A} \cdot B$$

- (c) Show the circuit -(don't build)

$$Y = (A \cdot B \cdot C) + D + E$$

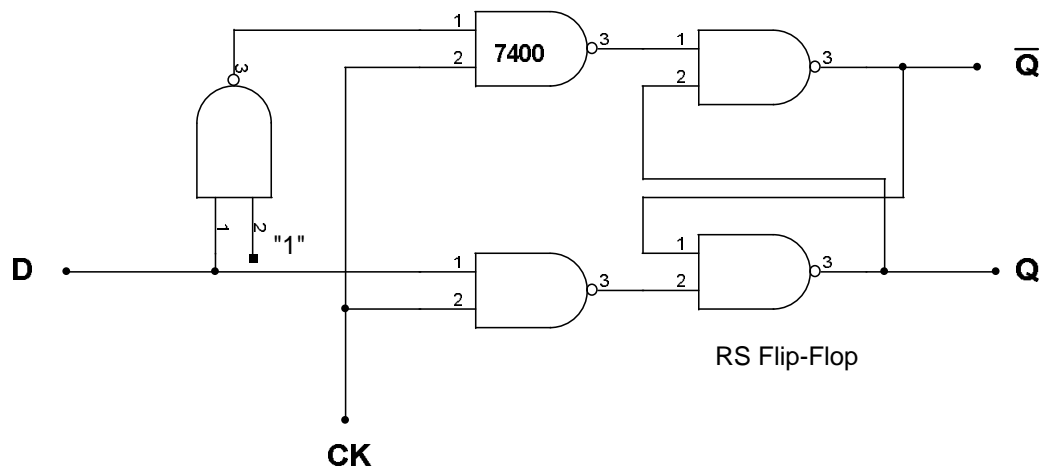3. Cross couple 2 NAND gates to make an RS flip-flop. Then add the gates to make a DATA flip-flop. Test its properties.




note: "1" means that this input should be held at the logical 1 level by connecting it to +5V.

- Verify the truth table for a JK flip-flop, using the 74LS112. (The Clock is CP). The data sheet for the out-dated 7473 flip-flop is included for its superior functional block diagram. Study it and see how a JKFF works.

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n


Here, J and K refer to the respective input levels when the n^{th} clock is high, and Q_{n+1} refers to the output after clock returns from 1 to 0. These flip-flops have a “set” (SD) and a “reset” (RD) feature. Experiment with the \bar{SD} and \bar{RD} inputs to determine their effect. See waveforms on pg 4-168 of the 74LS112 data sheet.

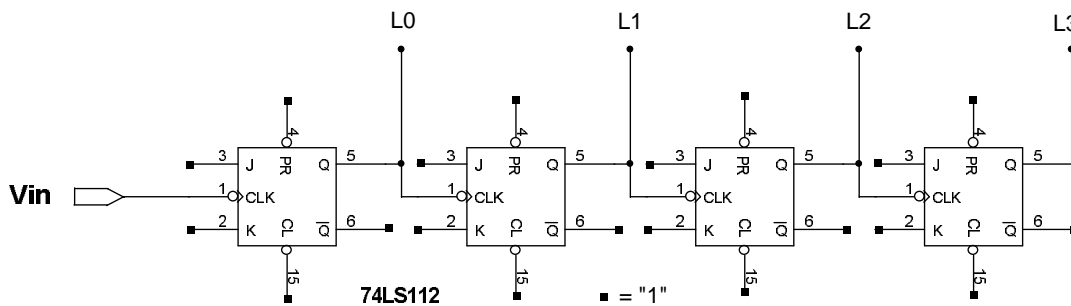- Connect the 74LS112 JKFF’s to make an 4 bit counter (0 to 15). To display the sequence of bits use the lights on the board. Don’t forget to hook up **all** the inputs, even if they aren’t shown on the functional logic diagram.



- Make a ring oscillator.

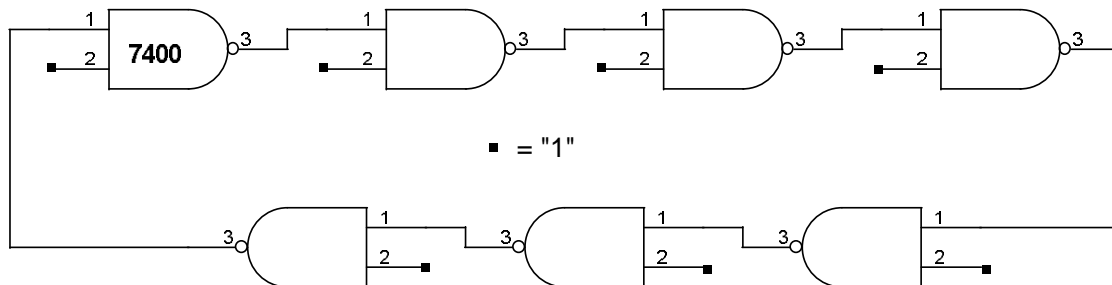Use an odd number of gates. A signal is propagated around the loop with a speed depending on the delay of each gate and the number of gates. For 7 gates the period is about 50 - 150 nsec., depending on the type of gate. Check the frequency by looking at the output of any gate with the scope. Use your four bit counter to count the oscillations.



Digital Circuits II

4 Purpose

- To continue the study of the basic principles of digital circuitry.
- To understand the operation of various special purpose gates and circuits.

5 Discussion

The circuits are logically TTL 74LS00 series from various manufacturers. A reminder that the logic levels are:


- **One:** 3 to 5.0 V; nominally 4.75 V.
- **Zero:** 0 to 0.4 V; nominally ground = 0 V.
- Switching Level ~ 1.4 V.

The delay in passing a signal through one NAND gate is typically 7-13 ns. However, depending on availability, you may be using a device which, although it has the same voltage and logic values as normal TTL, will differ in speed and input power required. For example “Schottky TTL” is distinguished by the LS notation and is significantly faster than the normal TTL. Some of the gates we are using in this lab are based on CMOS technology and are pin-for-pin compatible with TTL, denoted by the initials HCT preceding the chip number.

The fanout capability is usually 10, (i.e. ten inputs can be connected to each output). The detailed specifications of the individual chips are described in the attached sheets.

6 Procedure

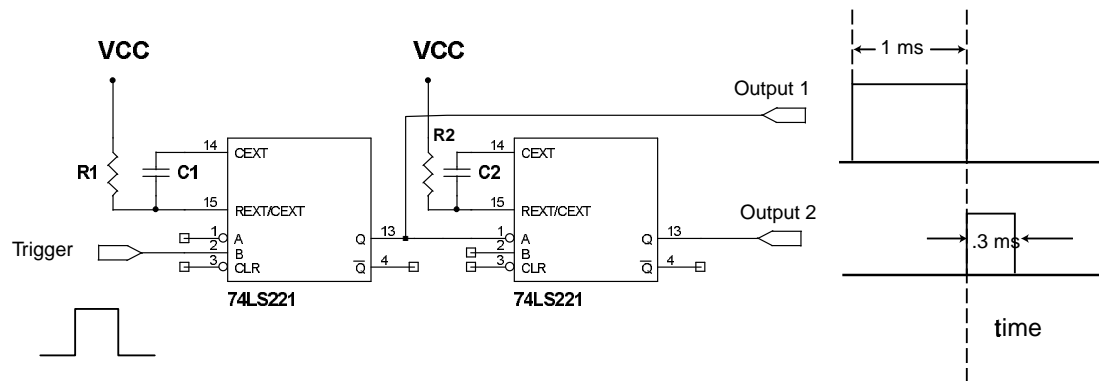1. Study the behavior of the monostable multivibrator (oneshot). A dual oneshot has an id number 74LS221. Connect the circuit shown. Check the spec sheet for valid resistor and capacitor values! Arrange the two outputs so that they have the appropriate relative timing when triggered by a rising edge. Determine the output pulse width relative to the RC time constant of your external circuit. What changes would have to be made to trigger your circuit on the falling edge? What would the result be if you used the rising-edge trigger input (B) on the second one-shot?



- Investigate the properties of the 8 bit serial-input parallel-output shift register (ID = 74HCT164). Connect the chip, then clock various numbers into the register using the switches. Use the eight LED's on the breadboard to show the states of the output. How does the "Reset" function work? Keep the circuit set up for the next exercise.
- The 74LS283 is a four bit adder which performs the binary addition of one 4 bit number (A_1 to A_4) to another (B_1 to B_4), including a "carry in" bit (C_0), in order to produce a 4-bit sum (S_1 to S_4) plus a "carry out" (C_4).
Use the shift register to generate both the input binary numbers, so that A_1 to A_4 correspond to Q_E through Q_H and B_1 to B_4 to Q_A through Q_D . For convenience it is useful to connect the input and output 4-bit numbers to a hex display using the TIL311 chip. Verify the addition.
- Replace the adder with a four bit magnitude comparator (74LS85). Compare the two displayed numbers and verify all the outputs. Now experiment with the carry inputs to determine what values are required to function correctly.

